

Chandler Bottomley  
2/11/20

In this lab we learned how to combine layouts. We also learned how to make the parasitic view of the schematics. We also learned how to make a ring oscillator.







